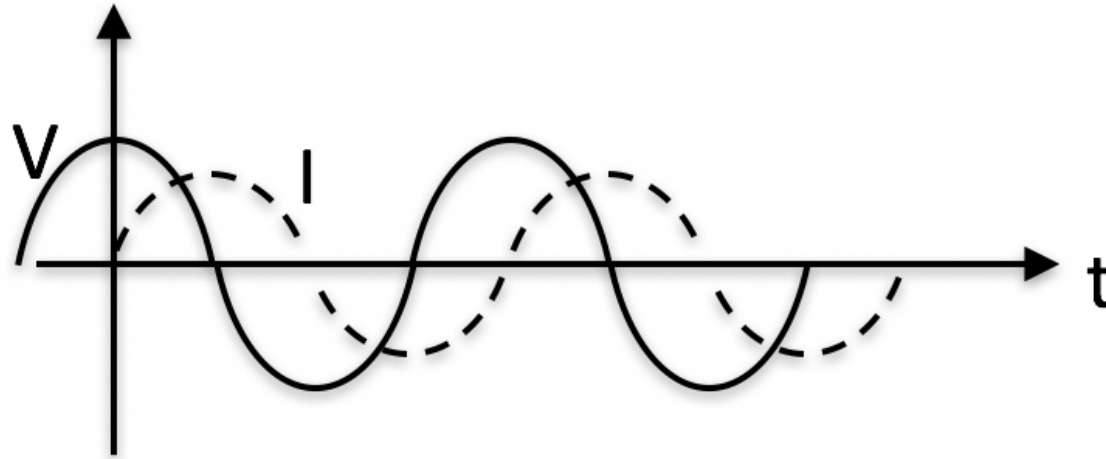


A capacitor (C) and an inductor (L) are in parallel. What is the effective impedance, Z_{eff} across these elements?

- A. $C + L$
- B. $i\omega C + i\omega L$
- C. $1/(i\omega C + i\omega L)$
- D. $1/i\omega C + i\omega L$
- E. Something else?

AC voltage V and current I vs time t are as shown:



The graph shows that..

- A. I leads V (I peaks before V peaks)
- B. I lags V (I peaks after V peaks)
- C. Neither

Suppose you have a circuit driven by a voltage:

$$V(t) = V_0 \cos(\omega t)$$

You observe the resulting current is:

$$I(t) = I_0 \cos(\omega t - \pi/4)$$

Would you say the current is

A. leading

B. lagging

the voltage by 45 degrees?

Consider an RC circuit attached to a sinusoidally driven voltage source. If at $t = 0$ we turn on the source,

$I(t = 0) = \frac{V_0}{R}$. Then the current follows this solution,

$$I(t) = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t + \phi) - \left(\frac{V_0}{R} - \frac{V_0 \cos \phi}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \right)$$

What happens to the long term current as $\omega \rightarrow 0$?

- A. goes to zero
- B. goes to $\frac{V_0}{R}$
- C. goes to infinity
- D. Something else

Consider an RC circuit attached to a sinusoidally driven voltage source. If at $t = 0$ we turn on the source,

$I(t = 0) = \frac{V_0}{R}$. Then the current follows this solution,

$$I(t) = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t + \phi) - \left(\frac{V_0}{R} - \frac{V_0 \cos \phi}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \right)$$

What happens to the long term current as $\omega \rightarrow \infty$?

- A. goes to zero
- B. goes to $\frac{V_0}{R}$
- C. goes to infinity
- D. Something else